



JYOTHY
INSTITUTE OF TECHNOLOGY


**DEPARTMENT OF COMPUTER SCIENCE &
ENGINEERING**

DIGITAL DESIGN & COA

INTEGRATED LABORATORY

REFERENCE GUIDE

BCS302

 

Prepared by:
Mr. Akhilesh S Narayan, B.E, MSE, DiMAP
Asst. Professor,
Dept. of CSE

★ **PROGRAM 1:** Given a 4-variable logic expression, simplify it using the appropriate technique and simulate the same using basic gates.

```
module four_var_logic (  
    input A,  
    input B,  
    input C,  
    input D,  
    output Y  
);  
  
    assign Y = (C & D) | (~A & D); //  $Y = CD + A'D$   
  
endmodule
```

- *Need to select any sample 4 variable expression, simplify it using K-Maps and then implement the simplified expression using Verilog.*
- *Using a test bench, you also need to test all possible combinations for the given variables.*

★ **PROGRAM 2:** Design a 4-bit full adder and subtractor and simulate the same using basic gates.

```
a) module FullAdder4bit (  
    input [3:0] A,  
    input [3:0] B,  
    input Cin,  
    output [3:0] Sum,  
    output Cout  
);  
    wire C1, C2, C3;  
  
    // 1st bit  
    FullAdder FA1(A[0], B[0], Cin, Sum[0], C1);  
    // 2nd bit
```

```
FullAdder FA2(A[1], B[1], C1, Sum[1], C2);  
// 3rd bit  
FullAdder FA3(A[2], B[2], C2, Sum[2], C3);  
// 4th bit  
FullAdder FA4(A[3], B[3], C3, Sum[3], Cout);  
  
endmodule
```

```
module FullAdder (  
    input A,  
    input B,  
    input Cin,  
    output Sum,  
    output Cout  
);  
  
assign Sum = A ^ B ^ Cin;  
assign Cout = (A & B) | (A & Cin) | (B & Cin);  
endmodule
```

```
b) module FullSubtractor4bit (  
    input [3:0] A,  
    input [3:0] B,  
    input Bin,  
    output [3:0] Diff,  
    output Bout  
);  
  
wire B1, B2, B3;  
  
// 1st bit  
FullSubtractor FS1(A[0], B[0], Bin, Diff[0], B1);  
// 2nd bit  
FullSubtractor FS2(A[1], B[1], B1, Diff[1], B2);  
// 3rd bit
```

```
FullSubtractor FS3(A[2], B[2], B2, Diff[2], B3);  
// 4th bit  
FullSubtractor FS4(A[3], B[3], B3, Diff[3], Bout);
```

```
endmodule
```

```
module FullSubtractor (  
    input A,  
    input B,  
    input Bin,  
    output Diff,  
    output Bout  
);
```

```
assign Diff = A ^ B ^ Bin;  
assign Bout = (~A & B & Bin) | (A & ~B & Bin);  
endmodule
```

★ **PROGRAM 3:** Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural models.

a. 2-input AND Gate, Structural Verilog:

```
module and_gate (  
    input a,  
    input b,  
    output y  
);
```

```
    assign y = a & b;
```

```
endmodule
```

Dataflow Verilog:

```
module and_gate (  
    input a,  
    input b,  
    output y  
);
```

```
    and (y, a, b);
```

```
endmodule
```

Behavioural Verilog:

```
module and_gate (  
    input a,  
    input b,  
    output y  
);
```

```
    assign y = (a == 1 && b == 1);
```

```
endmodule
```

b. 2-input XOR Gate, Structural Verilog:

```
module xor_gate (  
    input a,  
    input b,  
    output y  
);
```

```
    assign y = (a ^ b);
```

```
endmodule
```

Dataflow Verilog:

```
module xor_gate (  
    input a,  
    input b,  
    output y  
);  
  
    xor (y, a, b);  
  
endmodule
```

Behavioural Verilog:

```
module xor_gate (  
    input a,  
    input b,  
    output y  
);  
  
    assign y = (a != b);  
  
endmodule
```

c. 4-input Multiplexer, Structural Verilog:

```
module mux4to1 (  
    input sel,  
    input d0,  
    input d1,  
    input d2,  
    input d3,  
    output y  
);
```

```
assign y = (sel == 0) ? d0 : ((sel == 1) ? d1 : ((sel == 2) ? d2 : d3));
```

```
endmodule
```

Dataflow Verilog:

```
module mux4to1 (  
    input sel,  
    input d0,  
    input d1,  
    input d2,  
    input d3,  
    output y  
);
```

```
assign y = sel ? ((sel == 1) ? d1 : ((sel == 2) ? d2 : d3)) : d0;
```

```
endmodule
```

Behavioural Verilog:

```
module mux4to1 (  
    input sel,  
    input d0,  
    input d1,  
    input d2,  
    input d3,  
    output y  
);
```

```
case (sel)  
    0: assign y = d0;  
    1: assign y = d1;  
    2: assign y = d2;  
    default: assign y = d3;
```

```
endcase
```

```
endmodule
```

★ **PROGRAM 4:** Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.

```
module half_adder(  
    input A,  
    input B,  
    output sum,  
    output carry  
);
```

```
    assign sum = A ^ B;  
    assign carry = A & B;
```

```
endmodule
```

```
module full_adder(  
    input A,  
    input B,  
    input Cin,  
    output sum,  
    output Cout  
);
```

```
    wire sum1, carry1, carry2;
```

```
    half_adder HA1(A, B, sum1, carry1);  
    half_adder HA2(sum1, Cin, sum, carry2);  
    assign Cout = carry1 | carry2;
```

```
endmodule
```

```
module half_subtractor(  
    input A,  
    input B,  
    output difference,  
    output borrow  
);
```

```
    assign difference = A ^ B;  
    assign borrow = (~A & B);
```

```
endmodule
```

```
module full_subtractor(  
    input A,  
    input B,  
    input Bin,  
    output difference,  
    output Bout  
);
```

```
    wire diff1, bor1, bor2;
```

```
    half_subtractor HS1(A, B, diff1, bor1);  
    half_subtractor HS2(diff1, Bin, difference, bor2);  
    assign Bout = bor1 | bor2;
```

```
endmodule
```

```
module binary_adder_subtractor(  
    input [3:0] A,  
    input [3:0] B,  
    input SUB,  
    output [3:0] result,  
    output overflow  
);
```

```
wire [3:0] sum;
wire [3:0] difference;
wire carry_in, borrow_in, carry_out, borrow_out;

// Select adder or subtractor based on SUB signal
assign carry_in = ~SUB;
assign borrow_in = SUB;

// Instantiate full adders
full_adder FA0(A[0], B[0], carry_in, sum[0], carry_out);
full_adder FA1(A[1], B[1], carry_out, sum[1], carry_out);
full_adder FA2(A[2], B[2], carry_out, sum[2], carry_out);
full_adder FA3(A[3], B[3], carry_out, sum[3], carry_out);

// Instantiate full subtractors
full_subtractor FS0(A[0], B[0], borrow_in, difference[0], borrow_out);
full_subtractor FS1(A[1], B[1], borrow_out, difference[1], borrow_out);
full_subtractor FS2(A[2], B[2], borrow_out, difference[2], borrow_out);
full_subtractor FS3(A[3], B[3], borrow_out, difference[3], borrow_out);

// Assign result based on SUB signal
assign result = (SUB) ? difference : sum;

// Overflow detection
assign overflow = carry_out ^ borrow_out;

endmodule
```

★ **PROGRAM 5:** Design Verilog HDL to implement Decimal adder.

```
module DecimalAdder(
    input [3:0] A, // 4-bit input representing a decimal digit
    input [3:0] B,
    output reg [3:0] Sum
```

);

// Define constants for decimal to binary conversion

parameter [3:0] DECIMAL_TO_BINARY[9:0] = {4'b0000, 4'b0001, 4'b0010, 4'b0011, 4'b0100, 4'b0101, 4'b0110, 4'b0111, 4'b1000, 4'b1001};

// Define constants for binary to decimal conversion

parameter [3:0] BINARY_TO_DECIMAL[15:0] = {4'b0000, 4'b0001, 4'b0010, 4'b0011, 4'b0100, 4'b0101, 4'b0110, 4'b0111, 4'b1000, 4'b1001, 4'b0000, 4'b0000, 4'b0000, 4'b0000};

// Convert A and B to binary

reg [3:0] A_binary;

reg [3:0] B_binary;

always @(*) begin

 A_binary = DECIMAL_TO_BINARY[A];

 B_binary = DECIMAL_TO_BINARY[B];

end

// Perform binary addition

reg [4:0] binary_sum;

always @(*) begin

 binary_sum = A_binary + B_binary;

end

// Convert binary sum back to decimal

always @(*) begin

 Sum = BINARY_TO_DECIMAL[binary_sum];

end

endmodule

★ **PROGRAM 6:** Design a Verilog program to implement Different types of multiplexers like 2:1, 4:1 and 8:1.

a. 2:1 Multiplexer:

```
module mux2to1(  
    input a,  
    input b,  
    input sel,  
    output y  
);  
    assign y = (sel) ? b : a;  
  
endmodule
```

b. 4:1 Multiplexer:

```
module mux4to1(  
    input d0,  
    input d1,  
    input d2,  
    input d3,  
    input sel1,  
    input sel0,  
    output y  
);  
    assign y = (sel1 == 1'b1) ? ((sel0 == 1'b1) ? d3 : d1) : ((sel0 == 1'b1) ? d2 : d0);  
  
endmodule
```

c. 8:1 Multiplexer:

```
module mux8to1(  
    input d0,  
    input d1,  
    input d2,  
    input d3,  
    input d4,
```

```
    input d5,
    input d6,
    input d7,
    input sel2,
    input sel1,
    input sel0,
    output y
);
    assign y = (sel2 == 1'b1) ? ((sel1 == 1'b1) ? ((sel0 == 1'b1) ? d7 : d5) : ((sel0 == 1'b1)
? d6 : d4)) : ((sel1 == 1'b1) ? ((sel0 == 1'b1) ? d3 : d1) : ((sel0 == 1'b1) ? d2 : d0));

endmodule
```

★ **PROGRAM 7:** Design a Verilog program to implement types of De-Multiplexer.

a. 1:2 De-Multiplexer:

```
module demux1to2(
    input d,
    input sel,
    output y0,
    output y1
);

    assign y0 = ~sel & d;
    assign y1 = sel & d;

endmodule
```

b. 2:4 De-Multiplexer:

```
module demux2to4(
    input d0,
    input d1,
    output y0,
```

```
    output y1,  
    output y2,  
    output y3  
);  
  
    assign y0 = ~d1 & ~d0;  
    assign y1 = ~d1 & d0;  
    assign y2 = d1 & ~d0;  
    assign y3 = d1 & d0;  
  
endmodule
```

c. 3:8 De-Multiplexer:

```
module demux3to8(  
    input d0,  
    input d1,  
    input d2,  
    output y0,  
    output y1,  
    output y2,  
    output y3,  
    output y4,  
    output y5,  
    output y6,  
    output y7  
);  
  
    assign y0 = ~d2 & ~d1 & ~d0;  
    assign y1 = ~d2 & ~d1 & d0;  
    assign y2 = ~d2 & d1 & ~d0;  
    assign y3 = ~d2 & d1 & d0;  
    assign y4 = d2 & ~d1 & ~d0;  
    assign y5 = d2 & ~d1 & d0;  
    assign y6 = d2 & d1 & ~d0;
```

```
assign y7 = d2 & d1 & d0;
```

```
endmodule
```

★ **PROGRAM 8:** Design a Verilog program for implementing various types of Flip-Flops such as SR, JK and D.

1. SR Flip-Flop:

```
module sr_ff(  
    input clk,  
    input S,  
    input R,  
    output reg Q  
);  
  
    always @(posedge clk) begin  
        if (S && ~R) begin  
            Q <= 1'b1;  
        end else if (~S && R) begin  
            Q <= 1'b0;  
        end  
    end  
end  
  
endmodule
```

2. JK Flip-Flop:

```
module jk_ff(  
    input clk,  
    input J,  
    input K,  
    output reg Q  
);
```

```
always @(posedge clk) begin
    if (J && ~K) begin
        Q <= 1;
    end else if (~J && K) begin
        Q <= 0;
    end
end
end
```

```
endmodule
```

3. D Flip-Flop:

```
module d_ff(
    input clk,
    input D,
    output reg Q
);
```

```
always @(posedge clk) begin
    Q <= D;
end
```

```
endmodule
```

NOTE:

- *Practice all the experiments giving a variety of inputs to get familiar with the IDE.*
 - *Make the habit of reading the errors and debugging them. Scroll through the output window to get details of the errors.*
 - *Understand combinational and sequential logic properly to gain insights into the problem statement.*
-